

Optimization of CS SC Amplifier

Version 1

Christian Enz

2025-07-17

Table of contents

1	Introduction	3
2	Analysis	4
2.1	Small-signal Transfer Function	4
2.2	Minimum current for a given bandwidth (long-channel)	5
3	Design Example	9
3.1	Process	10
4	Simulation results from ngspice	13
4.1	Operating point	13
5	Conclusion	15
	References	16

1 Introduction

 


Figure 1.1: Schematic of the common-source switched-capacitor amplifier.

In this notebook, we want to minimize the bias current of the common-source (CS) closed-loop (CL) amplifier of Figure 1.1 for achieving a given gain and bandwidth.

2 Analysis

2.1 Small-signal Transfer Function

 


Figure 2.1: Small-signal schematic of the CS SC amplifier.

The small-signal schematic of the closed-loop common-source stage is shown in Figure 2.1. Notice that we added the input capacitance C_{in} which essentially corresponds to the transistor gate-to-source and gate-to-bulk capacitances. The gate-to-drain capacitance is included in C_F and therefore needs to be de-embedded in the design. It is easy to show that the transfer function is given by

$$A(s) \triangleq \frac{\Delta V_{out}}{\Delta V_{in}} = A_0 \cdot \frac{1 - s/\omega_z}{1 + s/\omega_p} \quad (2.1)$$

where

$$A_0 = A_{0,ideal} \cdot \frac{\beta \cdot A_{dc}}{1 + \beta \cdot A_{dc}} \cong A_{0,ideal} \quad \text{for } A_{dc} \gg 1, \quad (2.2)$$

$$A_{0,ideal} = -\frac{C_S}{C_F}, \quad (2.3)$$

$$\omega_p = \frac{1 + \beta \cdot A_{dc}}{R_{ds} \cdot C_{out}} \cong \frac{\beta \cdot A_{dc}}{R_{ds} \cdot C_{out}} = \frac{\beta \cdot G_m}{C_{out}}, \quad (2.4)$$

$$\omega_z = \frac{G_m}{C_F}. \quad (2.5)$$

 


Figure 2.2: Small-signal circuit to evaluate the feedback gain β .

$A_{dc} = G_m \cdot R_{ds}$ is the CS transistor DC voltage gain, $\beta \cdot A_{dc}$ the DC loop gain where β is the feedback gain which can be calculated from the schematic shown Figure 2.2 as

$$\beta \triangleq \frac{V}{V_{out}} = \frac{C_F}{C_F + C_S + C_{in}}. \quad (2.6)$$

The amplifier bandwidth is given by $\omega_c = \omega_p \cong \beta \cdot G_m / C_{out}$ where C_{out} is the total capacitance seen at the output

$$C_{out} = C_L + (1 - \beta) \cdot C_F = C_L + \frac{C_S + C_{in}}{C_F + C_S + C_{in}} \cdot C_F. \quad (2.7)$$

 


Figure 2.3: Small-signal transfer function of the CL CS amplifier.

In order to achieve some DC gain C_F is smaller than C_S and usually also smaller than C_L . This means that the right-hand side (RHS) zero is located higher than the unity gain frequency which is then simply given by $\omega_u \cong G_m / C_{out}$. For frequencies below ω_u , the magnitude of the transfer function is shown in Figure 2.3.

2.2 Minimum current for a given bandwidth (long-channel)

When optimizing the CL CS amplifier for low current consumption, the transistor is often biased in moderate or even weak inversion leading to large transistor and therefore an increased input and output capacitance. If we assume that the transistor parasitic capacitance at the drain is much smaller than the load capacitance, we can model this input capacitance as the sum of the gate-to-source and gate-to-bulk capacitances

$$C_{in} = C_{GS} + C_{GB}. \quad (2.8)$$

Assuming transistor is biased in saturation, we have

$$C_{GS} \cong W L C_{ox} \cdot c_{gsi} + C_{GSo} \cdot W \quad (2.9)$$

where c_{gsi} is the normalized intrinsic gate-to-source capacitance which is typically equal to 2/3 in strong inversion and is proportionnal to IC in weak inversion. C_{GSo} is the gate-to-source overlap capacitance per unit width.

The gate-to-bulk capacitance C_{GB} is given by

$$C_{GB} \cong W L C_{ox} \cdot c_{gbi} + C_{GBo} \cdot W, \quad (2.10)$$

where c_{gbi} is the normalized gate-to-bulk intrinsic capacitance which in strong inversion is given by

$$c_{gbi} = \frac{n - 1}{3n}. \quad (2.11)$$

C_{GBo} is the gate-to-bulk overlap capacitance per unit width.

For a given transistor length L , the input capacitance C_{in} scales with W according to

$$C_{in} = C_{GW} \cdot W, \quad (2.12)$$

where C_{GW} is the gate-to-source and gate-to-bulk capacitance per unit width given by

$$C_{GW} = L C_{ox} \cdot (c_{gsi} + c_{gbi}) + C_{GSo} + C_{GBo}. \quad (2.13)$$

In order to achieve a certain bandwidth we need to have a certain transconductance for a certain load capacitance. In order to maximize the current efficiency, we should bias the transistor in weak inversion. This leads to a large transistor and therefore large parasitic capacitances which will impact the bandwidth. Imposing the bandwidth, at some point the capacitance becomes so large that it is no more possible to achieve the required transconductance in weak inversion for the desired bandwidth. Does this mean that there is a minimum current for the CL CS amplifier to achieve a certain bandwidth?

To answer this question we need to solve the following set of equations for I_b and W assuming a given length L

$$\omega_c = \beta \cdot \frac{G_m}{C_{out}}, \quad (2.14)$$

$$C_{out} = C_L + (1 - \beta) \cdot C_F, \quad (2.15)$$

$$\beta = \frac{C_F}{C_F + C_S + C_{in}}, \quad (2.16)$$

$$C_{in} = W \cdot C_{GW}, \quad (2.17)$$

$$I_b = I_{spec\Box} \cdot \frac{W}{L} \cdot IC, \quad (2.18)$$

$$G_m = \frac{I_{spec\Box}}{nU_T} \cdot \frac{W}{L} \cdot g_{ms}(IC), \quad (2.19)$$

where $g_{ms}(IC)$ is the long-channel normalized source transconductance given by

$$g_{ms} = \frac{\sqrt{4IC + 1} - 1}{2} = \frac{2IC}{\sqrt{4IC + 1} + 1}. \quad (2.20)$$

Solving for I_b and W/L leads to the following normalized solutions

$$i_b \triangleq \frac{I_b}{I_{pec\Box} \cdot \Omega} = \frac{IC}{g_{ms}(IC) - \Theta}, \quad (2.21)$$

$$AR \triangleq \frac{W/L}{\Omega} = \frac{1}{g_{ms} - \Theta}, \quad (2.22)$$

where

$$\Omega \triangleq \frac{\omega_c}{\omega_L}, \quad (2.23)$$

$$\omega_L \triangleq \frac{I_{spec\Box}}{nU_T} \cdot \frac{1}{(1 + C_S/C_L + C_S/C_F) \cdot C_L}, \quad (2.24)$$

$$\Theta \triangleq \frac{\omega_c}{\omega_W}, \quad (2.25)$$

$$\omega_W \triangleq \frac{I_{spec\Box}}{nU_T} \cdot \frac{1}{(1 + C_L/C_F) \cdot C_{GW} \cdot L}. \quad (2.26)$$

The normalized current i_b is plotted below for different values of Θ .

From Figure 2.4, we clearly see that there is a minimum current for a given value of parameter Θ . We can find the optimum inversion coefficient IC_{opt} which is given by

$$IC_{opt} = \left(\sqrt{\Theta \cdot (1 + \Theta)} + \Theta + \frac{1}{2} \right)^2 - \frac{1}{4} \quad (2.27)$$

$$= 2\Theta \cdot (1 + \Theta) + (1 + 2\Theta) \cdot \sqrt{\Theta \cdot (1 + \Theta)} \quad (2.28)$$

$$\cong 2\Theta + \sqrt{\Theta} \text{ for } \Theta \ll 1. \quad (2.29)$$

 


Figure 2.4: Normalized bias current i_b versus inversion coefficient IC .

We also see that there is a minimum inversion coefficient IC_{lim} below which the desired bandwidth ω_c can no more be achieved

$$IC_{lim} = \Theta \cdot (1 + \Theta) \cong \Theta, \quad (2.30)$$

which is about equal to Θ for small values of Θ .

The optimum normalized current is given by

$$i_{b,opt} \triangleq i_b(IC_{opt}) = 1 + 2\Theta + 2\sqrt{\Theta \cdot (1 + \Theta)}. \quad (2.31)$$

The optimum current also corresponds an optimum transistor width W and hence an optimum normalized W/L given by

$$AR_{opt} \triangleq AR(IC_{opt}) = \frac{1}{\sqrt{\Theta \cdot (1 + \Theta)}}. \quad (2.32)$$

 


Figure 2.5: Normalized aspect ratio W/L versus inversion coefficient IC .

We see from Figure 2.5 that the transistor width increases first as $1/\sqrt{IC}$ in strong inversion and then as $1/IC$ in weak inversion making the transistor quickly very large until IC reaches IC_{lim} where the width becomes infinity. The dots correspond to the AR obtained for IC_{opt} .

3 Design Example

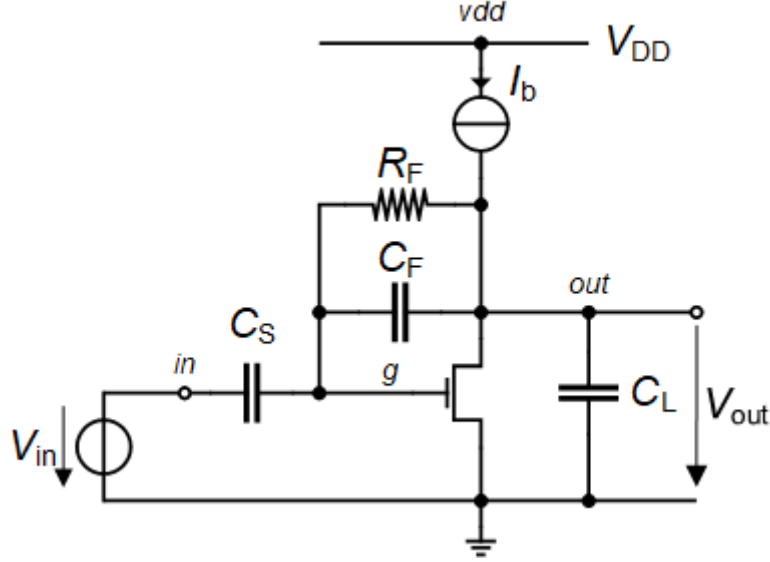


Figure 3.1: Schematic of the CS SC amplifier used for simulations.

We want to size a CS SC amplifier for the specifications given in Table 3.1. We need to find the minimum current and size the transistor to achieve this specs. We will design the amplifier for a generic 180nm bulk CMOS process. The physical parameters are given in Table 3.2, the global process parameters in Table 3.3 and finally the MOSFET parameters in Table 3.4.

Note that the feedback resistor R_F in Figure 3.1 has been added for biasing purpose and should be taken large enough not to limit the gain and bandwidth. The cut-off frequency due to R_F is given by

$$\omega_l = \frac{A_0}{R_F \cdot C_S} \quad (3.1)$$

from which we deduce the value of R_F

$$R_F = \frac{A_0}{\omega_l \cdot C_S}. \quad (3.2)$$

We will set f_l to 1 Hz.

Table 3.1: CS SC amplifier specifications.

Specification	Symbol	Value	Unit
DC gain	A_{dc}	20	dB
Bandwidth	BW	100	kHz
Load capacitance	C_L	1	pF
Feedback capacitance	C_F	100	fF
Transistor length	L	1	μm

3.1 Process

We will design the CS CL amplifier for generic 180nm bulk CMOS process. The physical parameters are given in Table 3.2, the global process parameters in Table 3.3 and finally the MOSFET parameters in Table 3.4.

Table 3.2: Physical parameters

Parameter	Value	Unit
T	300	K
U_T	25.875	mV

Table 3.3: Global process parameters

Parameter	Value	Unit
V_{DD}	1.8	V
C_{ox}	8.443	$\frac{fF}{\mu m^2}$
W_{min}	200	nm
L_{min}	180	nm

Table 3.4: Transistor process parameters

Parameter	NMOS	PMOS	Unit
sEKV parameters			
n	1.27	1.31	-
$I_{spec\Box}$	715	173	nA
V_{T0}	0.455	0.445	V
L_{sat}	26	36	nm
λ	20	20	$\frac{V}{\mu m}$
Overlap capacitances parameters			
C_{GDo}	0.366	0.329	$\frac{fF}{\mu m}$
C_{GSo}	0.366	0.329	$\frac{fF}{\mu m}$
C_{GBo}	0	0	$\frac{fF}{\mu m}$
Junction capacitances parameters			
C_J	1	1.121	$\frac{fF}{\mu m^2}$
C_{JSW}	0.2	0.248	$\frac{fF}{\mu m}$
Flicker noise parameters			
K_F	8.1e-24	8.1e-24	J
AF	1	1	-
ρ	0.05794	0.4828	$\frac{V \cdot m^2}{A \cdot s}$
Matching parameters			
A_{VT}	5	5	$mV \cdot \mu m$
A_β	1	1	$\% \cdot \mu m$
Source and drain sheet resistance parameter			
R_{sh}	600	2386	$\frac{\Omega}{\mu m}$
Width and length parameters			
ΔW	39	54	nm
ΔL	-76	-72	nm

We first need to estimate the parameter C_{GW} which is related to the transistor input capacitance C_{in} . Since we don't know the inversion coefficient we cannot estimate c_{gsi} and c_{gbi} . We therefore will take their values in strong inversion for the estimation of the input capacitance per width C_{GW}

$$C_{GW} \cong \left(1 - \frac{1}{3n}\right) \cdot C_{ox} \cdot L + C_{GS0} + C_{GB0}, \quad (3.3)$$

which depends on transistor length L . Since the above theory was developed for a long-channel device, we will choose $L = 1 \mu m$. We can now estimate the total gate capacitance per unit width for an n-channel transistor.

For the selected technology, we get $C_{GW} = 6.596 fF/\mu m$.

From the DC gain specification $A_0 = 10$, we get $C_S = 1 pF$. We can compute the optimum inversion coefficient IC_{opt} , optimum width W_{opt} , optimum current $I_{b,opt}$ and aspect ratio $W/L|_{opt}$ which are given in Table 3.5.

Table 3.5: CS SC amplifier optimum parameters.

Parameter	Value	Unit
A_0	10	-
C_S	1	pF
f_L	288.269	kHz
f_W	47.679	MHz
Ω	0.347	-
θ	0.002097	-
IC_{opt}	0.05	-
$i_{b,opt}$	1.096	-
AR_{opt}	21.813	-
$\left(\frac{W}{L}\right)_{opt}$	7.567	-
$I_{b,opt}$	272	nA
W_{opt}	7.57	μm
C_{in}	49.908	fF
C_{GD}	2.773	fF
C_F	100	fF
C_{F0}	97.227	fF
R_F	0.159	$T\Omega$

Table 3.6: Transistor size and bias information.

Transistor	$W [\mu m]$	$L [\mu m]$	$I_D [nA]$	$I_{spec} [nA]$	IC	$V_G - V_{T0} [mV]$	$V_{DSsat} [mV]$
M1	7.57	1.00	272	5410	0.050	-60	104

Table 3.7: Transistor small-signal and thermal noise parameters.

Transistor	$G_{spec} [\mu A/V]$	$G_{ms} [\mu A/V]$	$G_m [\mu A/V]$	$G_{ds} [nA/V]$	γ_n
M1	209.093	10.024	7.885	13.591	0.645

The transistor size and bias information are given in Table 3.6, while Table 3.7 gives the small-signal parameters.

 


Figure 3.2: Theoretical transfer function.

4 Simulation results from ngspice

The theoretical results can be validated by comparing them to the results obtained from simulations performed with ngspice. The cells below will run the simulations with ngspice. In order to run the simulations you need to have ngspice installed. Please refer to the ngspice instructions.

i Note

The simulations are performed with ngspice [1] using the EKV 2.6 compact model [2]. For ngspice, we use the original Verilog-A implementation of EKV 2.6 [3] modified by C. Enz to get the operating point informations and available on the Gitub va-models site provided by D. Warning at [4]. The parameters correspond to a generic 180 nm bulk CMOS process [5].

4.1 Operating point

Before running the AC simulation, we first need to check the quiescent voltages and currents and the operating point by running an .OP simulation. The node voltages are extracted from the .ic file and presented in Table 4.1.

Table 4.1: OTA node voltages with the OTA in open-loop without offset correction.

Node	Voltage
vdd	1.8
in	0
g	0.382048
out	0.382048

Table 4.2: PSP operating point information extracted from ngspice .op file for each transistor.

Transistor	I_D [nA]	I_{spec} [nA]	IC	n	V_{Dsat} [mV]
M1	274	6034	0.045	1.27	114

Table 4.3: PSP small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	n	G_{ms} [$\mu A/V$]	G_m [$\mu A/V$]	G_{mb} [$\mu A/V$]	G_{ds} [nA/V]
M1	1.27	10.145	7.835	2.292	17.705

The large-signal transistor bias information and the small-signal parameters extracted from the simulation are given in Table 4.2 and Table 4.3, respectively. We see that their values are very close to the theoretical values given in Table 3.6 and Table 3.7.

The simulated transfer function is shown in Figure 4.1 and compared to the theoretical transfer function of Figure 2.3. We see a perfect match between theory and simulation.

 


Figure 4.1: Simulated gain response compared to theoretical estimation.

5 Conclusion

In this notebook we have optimized a single transistor SC amplifier for minimum power consumption. We started to analyze the circuit accounting for the input parasitic capacitance which scales with the width of the transistor. We have found that there is an optimum transistor inversion coefficient and width for achieving a certain bandwidth with a minimum bias current. We then illustrated the theory with an example. The sized circuit was then simulated with ngspice using the EKV 2.6 compact model for a generic 180nm CMOS technology. The simulation results perfectly match the theory.

References

- [1] Holger Vogt, Giles Atkinson, Paolo Nenzi, “Ngspice User’s Manual Version 43.” <https://ngspice.sourceforge.io/docs/ngspice-43-manual.pdf>, 2024.
- [2] M. Bucher, C. Lallement, C. Enz, F. Théodoloz, and F. Krummenacher, “The EPFL-EKV MOSFET Model Equations for Simulation.” https://github.com/chrisenz/EKV/blob/main/EKV2.6/docs/ekv_v26_rev2.pdf, 1998.
- [3] W. Grabinski *et al.*, “FOSS EKV2.6 verilog-a compact MOSFET model,” in *European solid-state device research conference (ESSDERC)*, 2019, pp. 190–193. doi: [10.1109/ESSDERC.2019.8901822](https://doi.org/10.1109/ESSDERC.2019.8901822).
- [4] Dietmar Warning, “Verilog-A Models for Circuit Simulation.” <https://github.com/dwarning/VA-Models>, 2024.
- [5] W. Grabinski *et al.*, “FOSS EKV 2.6 parameter extractor,” in *2015 22nd international conference mixed design of integrated circuits & systems (MIXDES)*, 2015, pp. 181–186. doi: [10.1109/MIXDES.2015.7208507](https://doi.org/10.1109/MIXDES.2015.7208507).