

# **Design of the Folded Cascode OTA**

**For a Generic 180nm Bulk CMOS Process (Version 2)**

Christian Enz ([christian.enz@epfl.ch](mailto:christian.enz@epfl.ch))

2025-07-25

# Table of contents

<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>Analysis</b>	<b>5</b>
2.1	Small-signal analysis . . . . .	5
2.2	Noise Analysis . . . . .	5
2.2.1	Input-referred thermal noise . . . . .	6
2.2.2	Input-referred flicker noise . . . . .	6
2.3	Input-referred offset voltage . . . . .	7
<b>3</b>	<b>Design</b>	<b>9</b>
3.1	Specifications . . . . .	9
3.2	Process . . . . .	9
3.3	Design procedure . . . . .	10
3.3.1	Sizing the differential pair $M_{1a}$ - $M_{1b}$ . . . . .	11
3.4	Sizing of $M_{3a}$ - $M_{3b}$ . . . . .	11
3.5	Sizing of $M_{4a}$ - $M_{4b}$ and $M_{5a}$ - $M_{5b}$ . . . . .	13
3.6	Sizing of $M_{2a}$ - $M_{2b}$ - $M_{2c}$ . . . . .	14
3.7	Sizing $M_{7a}$ - $M_{7b}$ . . . . .	14
3.8	Bias voltages $V_{b1}$ and $V_{b2}$ . . . . .	15
3.9	Summary . . . . .	16
3.9.1	Specifications . . . . .	16
3.9.2	Bias . . . . .	16
3.9.3	Transistor information . . . . .	16
<b>4</b>	<b>OTA Characteristics</b>	<b>18</b>
4.1	Open-loop gain . . . . .	18
4.2	Input-referred noise . . . . .	19
4.3	Input-referred offset . . . . .	20
4.4	Current and power consumption . . . . .	21
<b>5</b>	<b>Simulation results from ngspice</b>	<b>23</b>
5.1	Operating point . . . . .	23
5.2	Large-signal differential transfer characteristic . . . . .	25
5.3	Open-loop gain . . . . .	27
5.4	Input-referred noise . . . . .	27
5.5	Input common-mode voltage range . . . . .	30
5.6	Step-response . . . . .	30
5.6.1	Small-step . . . . .	30
5.6.2	Large step . . . . .	31
5.7	Current and power consumption . . . . .	32
<b>6</b>	<b>Conclusion</b>	<b>33</b>
	<b>References</b>	<b>34</b>

# 1 Introduction

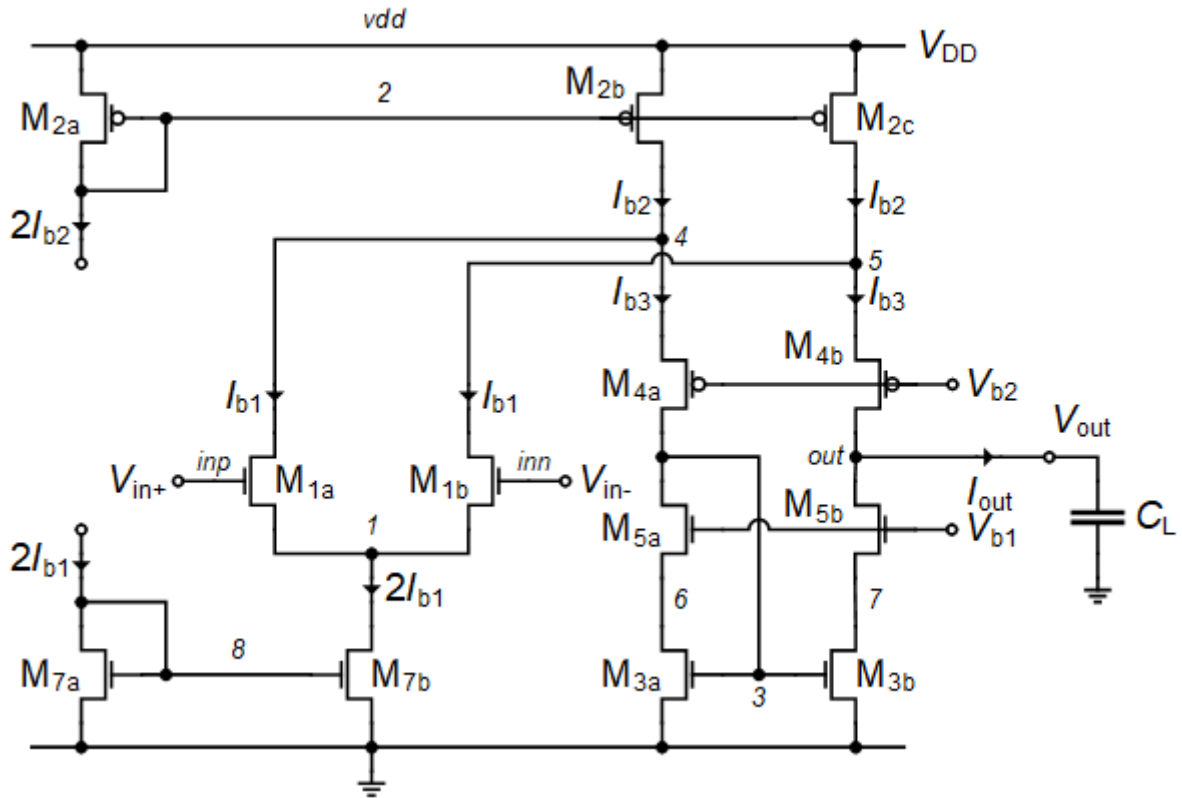


Figure 1.1: Schematic of the folded cascode differential OTA [1].

**i** Note

Note that all nMOS transistors in Figure 1.1 have an odd number and all the pMOS transistors an even number which explains the numbering process (this is the reason why there is no  $M_6$  transistor!).

This notebook presents the design of the folded cascode differential OTA [1] shown in Figure 1.1 for the same specifications used for the other OTAs. The folded cascode OTA is similar to the telescopic OTA except that the current  $I_{b3}$  flowing in the current mirror  $M_{3a}$ - $M_{3b}$  can be different than the current  $I_{b1}$  flowing in the differential pair. How to choose the ratio  $\alpha \triangleq I_{b3}/I_{b1}$ ? If the current  $I_{b3}$  is made equal to current  $I_{b1}$  ( $\alpha = 1$ ), then if the differential input voltage is largely positive, the differential pair will saturate and all the bias current  $2 I_{b1}$  is then steered into  $M_{1a}$ . This means that all the bias current  $I_{b2}$  is flowing into  $M_{1a}$  and no current is available at the input of the cascode current mirror  $M_{3a}$ - $M_{3b}$ . This situation should be avoided because it introduces an additional delay to charge the parasitic capacitance at node 3 and bring the current mirror  $M_{3a}$ - $M_{3b}$  back to normal operation. Usually, the ratio  $\alpha$  is taken  $1.2 < \alpha < 2$ . In order to minimize the current consumption, we will choose  $\alpha = 1.2$ . This means that the folded cascode OTA unavoidably consumes more current than the telescopic OTA (more than twice).

We will start with a detailed analysis of the OTA which will allow to derive all the design equations that will be used in the design phase. The OTA is then designed for a given set of specifications for a

generic 180 nm bulk CMOS technology. The design is then validated by simulations with ngspice [2] using the EKV 2.6 compact model [3] [4] [5] [6] with parameters corresponding to a generic 180 nm bulk CMOS technology [7] [8].

We now start with the small-signal analysis.

## 2 Analysis

### 2.1 Small-signal analysis

In a 1<sup>st</sup>-order analysis, we can neglect the capacitances at the low impedance cascode nodes 4, 5, 6 and 7 and only account for the capacitances at high impedance nodes 3 (gate of current mirror M<sub>3a</sub>-M<sub>3b</sub>) and out (output node). The circuit becomes similar to that of the simple OTA, with the dominant pole  $\omega_0$  at the output node (out) and the non-dominant pole  $\omega_p$  at the current mirror node 3. The transfer function also has a pole-zero doublet. Its transfer function is then given by

$$A_{dm}(s) \triangleq \frac{\Delta V_{out}}{\Delta V_{in}} \cong A_{dc} \cdot \frac{1 + s/\omega_z}{(1 + s/\omega_0)(1 + s/\omega_p)} \cong \frac{A_{dc}}{1 + s/\omega_0} \cong \frac{\omega_u}{s}, \quad (2.1)$$

where

$$A_{dc} \cong \frac{G_{m1}}{G_o}, \quad (2.2)$$

$$G_o \cong \frac{G_{ds3} G_{ds5}}{G_{ms5}} + \frac{(G_{ds1} + G_{ds2}) G_{ds4}}{G_{ms4}}, \quad (2.3)$$

$$\omega_0 \cong \frac{G_o}{C_L}, \quad (2.4)$$

$$\omega_p \cong \frac{G_{m3}}{C_3}, \quad (2.5)$$

$$\omega_z = 2\omega_p, \quad (2.6)$$

$$\omega_u = A_{dc} \cdot \omega_0 \cong \frac{G_{m1}}{C_L}. \quad (2.7)$$

### 2.2 Noise Analysis

At low-frequency the noise of the cascode transistors M<sub>4a</sub>-M<sub>4b</sub> and M<sub>5a</sub>-M<sub>5b</sub> can be neglected and the noise analysis is then identical to that of the simple OTA. The PSD of the output noise current is given by

$$S_{nout} \cong 2(S_{I_{n1}} + S_{I_{n2}} + S_{I_{n3}}) \quad (2.8)$$

which can be expressed in terms of the output noise conductance

$$S_{nout} = 4kT \cdot G_{nout}, \quad (2.9)$$

where

$$G_{nout} \cong 2(G_{n1} + G_{n2}G_{n3}), \quad (2.10)$$

with

$$G_{ni} = \gamma_{ni} \cdot G_{mi} + G_{mi}^2 \cdot \frac{\rho_i}{W_i L_i f} \quad \text{for } i = 1, 2, 3. \quad (2.11)$$

The input-referred noise resistance is then given by

$$R_{nin} \triangleq \frac{G_{nout}}{G_{m1}^2} = \frac{2(G_{n1} + G_{n2} + G_{n3})}{G_{m1}^2} = \frac{2G_{n1}}{G_{m1}^2} \cdot \left(1 + \frac{G_{n2}}{G_{n1}} + \frac{G_{n3}}{G_{n1}}\right) \quad (2.12)$$

which we rewrite as

$$R_{nin} = \frac{2 G_{n1}}{G_{m1}^2} \cdot (1 + \eta) \quad (2.13)$$

with

$$\eta = \frac{G_{n2}}{G_{n1}} + \frac{G_{n3}}{G_{n1}}. \quad (2.14)$$

$\eta$  represents the contribution of the current source  $M_{2b}$ - $M_{2c}$  and the current mirror  $M_{3a}$ - $M_{3b}$  referred to the input and normalized to the contribution of the differential pair  $M_{1a}$ - $M_{1b}$ . Of course during the design phase we will try to minimize  $\eta$ .

### 2.2.1 Input-referred thermal noise

The input-referred thermal noise resistance is given by

$$R_{nth} = \frac{2 \gamma_{n1}}{G_{m1}} \cdot (1 + \eta_{th}), \quad (2.15)$$

where

$$\eta_{th} = \frac{\gamma_{n2}}{\gamma_{n1}} \cdot \frac{G_{m2}}{G_{m1}} + \frac{\gamma_{n3}}{\gamma_{n1}} \cdot \frac{G_{m3}}{G_{m1}} \quad (2.16)$$

represents the contribution to the input-referred thermal noise of the current source  $M_{2b}$ - $M_{2c}$  and the current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair  $M_{1a}$ - $M_{1b}$ . In case  $G_{m1} \gg G_{m2}$  and  $G_{m1} \gg G_{m3}$ , then  $\eta_{th} \ll 1$  and the thermal noise is dominated by the input differential pair. Eqn. (2.15) can then be simplified to

$$R_{nth} \cong \frac{2 \gamma_{n1}}{G_{m1}}. \quad (2.17)$$

The OTA thermal noise excess factor is defined as

$$\gamma_{ota} \triangleq G_m \cdot R_{nth} \quad (2.18)$$

with  $G_m = G_{m1}$  the OTA equivalent transconductance. The OTA thermal noise excess factor then writes

$$\gamma_{ota} = 2 \gamma_{n1} \cdot (1 + \eta_{th}). \quad (2.19)$$

In the case  $G_{m1} \gg G_{m2}$  and  $G_{m1} \gg G_{m3}$ , then  $\eta_{th} \ll 1$  and the noise is dominated by the input differential pair  $M_{1a}$ - $M_{1b}$ . The OTA thermal noise excess factor can then be simplified as

$$\gamma_{ota} \cong 2 \gamma_{n1}. \quad (2.20)$$

### 2.2.2 Input-referred flicker noise

The input-referred flicker noise is given by

$$R_{nfl} = \frac{2}{f} \left[ \frac{\rho_n}{W_1 L_1} + \left( \frac{G_{m2}}{G_{m1}} \right)^2 \frac{\rho_p}{W_2 L_2} + \left( \frac{G_{m3}}{G_{m1}} \right)^2 \frac{\rho_n}{W_3 L_3} \right] \quad (2.21)$$

which can be rewritten as

$$R_{nfl} = \frac{2 \rho_n}{W_1 L_1 f} \cdot (1 + \eta_{fl}) \quad (2.22)$$

where

$$\eta_{fl} = \frac{\rho_p}{\rho_n} \left( \frac{G_{m2}}{G_{m1}} \right)^2 \frac{W_1 L_1}{W_2 L_2} + \left( \frac{G_{m3}}{G_{m1}} \right)^2 \frac{W_1 L_1}{W_3 L_3} \quad (2.23)$$

represents the contribution to the input-referred flicker noise of the current source  $M_{2b}$ - $M_{2c}$  and the current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair  $M_{1a}$ - $M_{1b}$ .

The corner frequency is the frequency at which the flicker noise becomes equal to the thermal noise

$$R_{nfl}(f = f_k) = R_{nth} \quad (2.24)$$

which is given by

$$f_k = \frac{1}{R_{nth}} \cdot \frac{2\rho_n}{W_1 L_1} \cdot (1 + \eta_{fl}) = \frac{G_{m1} \rho_n}{\gamma_{n1} W_1 L_1} \cdot \frac{1 + \eta_{fl}}{1 + \eta_{th}}. \quad (2.25)$$

The transconductance  $G_{m1}$  is set by the constraints either on thermal noise or on bandwidth (GBW product). The corner frequency  $f_k$  can be reduced by increasing  $W_1 L_1$  but also  $W_2 L_2$  and  $W_3 L_3$  at the same time to conserve the same  $\eta_{fl}$  factor. Assuming that  $G_{m2}/G_{m1} \ll 1$  and  $G_{m1} \gg G_{m3}$ , as required by the constraints on minimizing the contribution of the current source  $M_{2b}$ - $M_{2c}$  and current mirror  $M_{3a}$ - $M_{3b}$  to the input-referred offset and thermal noise, then  $\eta_{th} \ll 1$  and  $\eta_{fl} \ll 1$  and the corner frequency  $f_k$  is then mainly set by the differential pair transconductance and gate transistor area

$$f_k \cong \frac{G_{m1} \rho_n}{\gamma_{n1} W_1 L_1}. \quad (2.26)$$

## 2.3 Input-referred offset voltage

The offset analysis is similar to that of the simple OTA because the contribution of the mismatch of the cascode transistors can be neglected. The random offset current is then mainly due to the mismatch between  $M_{1a}$  and  $M_{1b}$ ,  $M_{2b}$  and  $M_{2c}$  and  $M_{3a}$  and  $M_{3b}$ . The variance of the output offset current is then given by

$$\sigma_{I_{os}}^2 \cong \sigma_{\Delta I_{D1}}^2 + \sigma_{\Delta I_{D2}}^2 + \sigma_{\Delta I_{D3}}^2 = I_{b1}^2 \cdot \sigma_{\frac{\Delta I_{D1}}{I_{D1}}}^2 + I_{b2}^2 \cdot \sigma_{\frac{\Delta I_{D2}}{I_{D2}}}^2 + I_{b3}^2 \cdot \sigma_{\frac{\Delta I_{D3}}{I_{D3}}}^2, \quad (2.27)$$

with

$$\sigma_{\frac{\Delta I_{Di}}{I_{Di}}}^2 = \sigma_{\beta_i}^2 + \left( \frac{G_{mi}}{I_b} \right)^2 \sigma_{V_{Ti}}^2 \quad \text{for } i = 1, 2, 3, \quad (2.28)$$

where

$$\sigma_{\beta_i}^2 = \frac{A_{\beta}^2}{W_i L_i} \quad \text{for } i = 1, 2, 3 \quad (2.29)$$

are the  $\beta$ -mismatches and

$$\sigma_{V_{Ti}}^2 = \frac{A_{V_T}^2}{W_i L_i} \quad \text{for } i = 1, 2, 3 \quad (2.30)$$

are the  $V_T$ -mismatches.

The variance of the output offset current then becomes

$$\sigma_{I_{os}}^2 = I_{b1}^2 \cdot \sigma_{\beta_1}^2 + I_{b2}^2 \cdot \sigma_{\beta_2}^2 + I_{b3}^2 \cdot \sigma_{\beta_3}^2 + G_{m1}^2 \cdot \sigma_{V_{T1}}^2 + G_{m2}^2 \cdot \sigma_{V_{T2}}^2 + G_{m3}^2 \cdot \sigma_{V_{T3}}^2. \quad (2.31)$$

The variance of the input-referred offset voltage is obtained by dividing the variance of the output offset current by  $G_{m1}^2$  resulting in

$$\sigma_{V_{os}}^2 = \sigma_{V_T}^2 + \sigma_{\beta}^2. \quad (2.32)$$

$\sigma_{V_T}^2$  is the  $V_T$ -mismatch given by

$$\sigma_{V_T}^2 = \sigma_{V_{T1}}^2 \cdot (1 + \xi_{V_T}) \quad (2.33)$$

where

$$\xi_{V_T} = \left( \frac{G_{m2}}{G_{m1}} \right)^2 \cdot \frac{\sigma_{V_{T2}}^2}{\sigma_{V_{T1}}^2} + \left( \frac{G_{m3}}{G_{m1}} \right)^2 \cdot \frac{\sigma_{V_{T3}}^2}{\sigma_{V_{T1}}^2} \quad (2.34)$$

represents the  $V_T$ -mismatch contributions to the input-referred offset of the current source  $M_{2b}$ - $M_{2c}$  and current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair with

$$\sigma_{V_{T1}} = \frac{A_{V_{Tn}}^2}{W_1 L_1}, \quad (2.35)$$

$$\sigma_{V_{T2}} = \frac{A_{V_{Tp}}^2}{W_2 L_2}, \quad (2.36)$$

$$\sigma_{V_{T3}} = \frac{A_{V_{Tn}}^2}{W_3 L_3}, \quad (2.37)$$

$\sigma_\beta^2$  is the  $\beta$ -mismatch given by

$$\sigma_\beta^2 = \left( \frac{I_{b1}}{G_{m1}} \right)^2 \cdot \sigma_{\beta_1}^2 \cdot (1 + \xi_\beta) \quad (2.38)$$

where

$$\xi_\beta = \left( \frac{I_{b2}}{I_{b1}} \right)^2 \frac{\sigma_{\beta_2}^2}{\sigma_{\beta_1}^2} + \left( \frac{I_{b3}}{I_{b1}} \right)^2 \frac{\sigma_{\beta_3}^2}{\sigma_{\beta_1}^2} \quad (2.39)$$

represents the  $\beta$ -mismatch contributions to the input-referred offset of the current source  $M_{2b}$ - $M_{2c}$  and current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair with

$$\sigma_{\beta_1}^2 = \frac{A_{\beta_n}^2}{W_1 L_1}, \quad (2.40)$$

$$\sigma_{\beta_2}^2 = \frac{A_{\beta_p}^2}{W_2 L_2}, \quad (2.41)$$

$$\sigma_{\beta_3}^2 = \frac{A_{\beta_n}^2}{W_3 L_3}. \quad (2.42)$$

Replacing in (2.34) and (2.39) results in

$$\xi_{V_T} = \left( \frac{G_{m2}}{G_{m1}} \right)^2 \left( \frac{A_{V_{Tp}}}{A_{V_{Tp}}} \right)^2 \frac{W_1 L_1}{W_2 L_2} + \left( \frac{G_{m3}}{G_{m1}} \right)^2 \frac{W_1 L_1}{W_3 L_3} \quad (2.43)$$

and

$$\xi_\beta = \left( \frac{I_{b2}}{I_{b1}} \right)^2 \left( \frac{A_{\beta_p}}{A_{\beta_n}} \right)^2 \frac{W_1 L_1}{W_2 L_2} + \left( \frac{I_{b3}}{I_{b1}} \right)^2 \frac{W_1 L_1}{W_2 L_2}. \quad (2.44)$$

Similarly to the flicker noise, the input-referred offset (variance or standard deviation) can be reduced by increasing the area  $W_1 L_1$  of  $M_{1a}$ - $M_{1b}$  but at the same time also increasing the area  $W_2 L_2$  of the current source  $M_{2b}$ - $M_{2c}$  and also the area  $W_3 L_3$  of the current mirror  $M_{3a}$ - $M_{3b}$ .



## 3 Design

### 3.1 Specifications

The OTA specifications are given in Table 3.1.

#### **i** Note

The specifications given in Table 3.1 are simplified specifications. They are mainly targeting the achievement of a certain gain-bandwidth product  $GBW$  and DC gain at lowest current consumption. The  $GBW$  sets the differential pair transconductance while the DC gain sets the output conductance. There is an additional specification on the random input-referred offset voltage which, if not met, might eventually require to increase the transistors area. There are no specifications on thermal noise since the transconductance is set by the  $GBW$ . There are no specifications on the flicker noise but if the corner frequency was set lower this would require to increase the transistors area. There are also no specifications on the slew-rate, which might be small because of the low-power objective. Finally, there are many more specifications such as CMRR, PSRR, input common-mode voltage range, output-voltage swing, etc. . . that are not discussed in this example.

Table 3.1: OTA specifications.

Specification	Symbol	Value	Unit
Minimum DC gain	$A_{dc}$	100	$dB$
Minimum gain-bandwidth product	$GBW$	1	$MHz$
Load capacitance	$C_L$	1	$pF$
Maximum input-referred random offset voltage	$V_{os}$	10	$mV$
Phase margin	$PM$	60	$^\circ$

### 3.2 Process

We will design the cascode gain stage for a generic 180nm bulk CMOS process. The physical parameters are given in Table 3.2, the global process parameters in Table 3.3 and finally the MOSFET parameters in Table 3.4.

Table 3.2: Physical parameters

Parameter	Value	Unit
$T$	300	$K$
$U_T$	25.875	$mV$

Table 3.3: Global process parameters

Parameter	Value	Unit
$V_{DD}$	1.8	$V$
$C_{ox}$	8.443	$\frac{fF}{\mu m^2}$
$W_{min}$	200	$nm$
$L_{min}$	180	$nm$

Table 3.4: Transistor process parameters

Parameter	NMOS	PMOS	Unit
sEKV parameters			
$n$	1.27	1.31	-
$I_{spec\Box}$	715	715	$nA$
$V_{T0}$	0.455	0.445	$V$
$L_{sat}$	26	36	$nm$
$\lambda$	20	20	$\frac{V}{\mu m}$
Overlap capacitances parameters			
$C_{GDo}$	0.366	0.329	$\frac{fF}{\mu m}$
$C_{GSo}$	0.366	0.329	$\frac{fF}{\mu m}$
$C_{GBo}$	0	0	$\frac{fF}{\mu m}$
Junction capacitances parameters			
$C_J$	1	1.121	$\frac{fF}{\mu m^2}$
$C_{JSW}$	0.2	0.248	$\frac{fF}{\mu m}$
Flicker noise parameters			
$K_F$	8.1e-24	8.1e-24	$J$
$AF$	1	1	-
$\rho$	0.05794	0.4828	$\frac{V \cdot m^2}{A \cdot s}$
Matching parameters			
$A_{VT}$	5	5	$mV \cdot \mu m$
$A_\beta$	1	1	$\% \cdot \mu m$
Source and drain sheet resistance parameter			
$R_{sh}$	600	2386	$\frac{\Omega}{\mu m}$
Width and length parameters			
$\Delta W$	39	54	$nm$
$\Delta L$	-76	-72	$nm$

### 3.3 Design procedure

#### ! Important

For this process, the transistor dimensions are rounded to 10nm. We also will ignore the length and width reduction parameters  $DL$  and  $DW$ . The main reason is that most of the transistor length and width are sufficiently large that ignoring these parameters has little impact.

We start sizing the differential pair  $M_{1a}$ - $M_{1b}$ .

### 3.3.1 Sizing the differential pair M<sub>1a</sub>-M<sub>1b</sub>

In this example there is no specification on the thermal noise. Therefore the transconductance  $G_{m1}$  is set by the gain-bandwidth product according to

$$GBW = \frac{G_{m1}}{2\pi C_{out}}, \quad (3.1)$$

where  $G_{m1}$  is the gate transconductance of M<sub>1a</sub> and M<sub>1b</sub> and  $C_{out}$  the total output capacitance

$$C_{out} = C_o + C_L \quad (3.2)$$

with  $C_o$  the parasitic capacitance at the output node and  $C_L$  the load capacitance.

In order to minimize the input-referred noise and offset, the input differential pair should be biased in weak inversion. The transconductance  $G_{m1}$  in deep weak inversion is then given by

$$G_{m1} = \frac{I_{b1}}{nU_T}. \quad (3.3)$$

The bias current  $I_{b1}$  is the current flowing in each transistor M<sub>1a</sub> and M<sub>1b</sub> when the input differential voltage is zero. The bias current provided by M<sub>5b</sub> is therefore  $2I_{b1}$ . The bias current must satisfy the following inequality:

$$I_{b1} \geq 2\pi n_{0n} U_T C_{out} GBW_{min}. \quad (3.4)$$

which for the given specifications gives  $I_{b1,min} = 207 \text{ nA}$ . The corresponding slew-rate is then equal to  $SR_{min} = 207 \text{ mV}/\mu\text{s}$  which we will consider as sufficient.

#### ! Important

If the slew-rate is not sufficient, the bias current  $I_b$  should be increased resulting in a higher current and power consumption. Other options include the use of a class AB OTA [9] or a dynamic/adaptive biasing OTA [10].

To have some margin to account for the additional parasitic capacitance at the output  $C_o$  due mostly to the junction capacitances that add to the load capacitance  $C_L$ , we set  $I_{b1} = 250 \text{ nA}$  and the inversion coefficient to  $IC_1 = 0.1$ . The transconductance can be calculated from the  $G_m/I_D$  function as  $G_{m1} = 6.962 \mu\text{A}/\text{V}$ . This leads to a gain-bandwidth product  $GBW = 1.1 \text{ MHz}$ , which is slightly higher than the target specification offering some margin. Knowing the drain current  $I_{D1}$  and the inversion coefficient, we can calculate the specific current  $I_{spec1} = 2.500 \mu\text{A}$  and the aspect ratio  $W_1/L_1 = 3.5$ .

The degree of freedom left ( $W_1$  or  $L_1$ ) can be determined by constraints either on the dc gain, the offset voltage or the flicker noise.

Before finalizing the sizing of the differential pair, we first will size the current mirror M<sub>3a</sub>-M<sub>3b</sub> and the current sources M<sub>2a</sub>-M<sub>2b</sub>-M<sub>2c</sub>.

### 3.4 Sizing of M<sub>3a</sub>-M<sub>3b</sub>

The current mirror M<sub>3a</sub>-M<sub>3b</sub> should be biased as much in strong inversion as the voltage constraint allows for. We can set its  $V_{GS}$  voltage to the desired quiescent output voltage which we set to  $V_{GS3} = V_{outq} = V_{DD}/2 = 900 \text{ mV}$ , which corresponds to an inversion coefficient  $IC_3 = 40.429$  and a saturation voltage  $V_{DSsat3} = 345 \text{ mV}$ . We see that choosing a large  $IC$  and hence a large  $V_{GS}$  voltage comes at the cost of a large saturation voltage and hence a reduced output voltage swing. As discussed in the introduction we have chosen  $\alpha = 1.200$  so that  $I_{b3} = 300 \text{ nA}$  and  $I_{b2} = I_{b1} + I_{b3} = 550 \text{ nA}$ . Having set the inversion coefficient and bias current we can derive the specific current  $I_{spec3} = 7.42$

$nA$  and the aspect ratio  $W_3/L_3 = 0.010$ . Having  $IC$  and  $I_D$ , we can deduce the transconductance  $G_{m3} = 1.326 \mu A/V$ .

We will now have to make sure that the non-dominant pole  $f_p$  at node 3 is sufficiently higher than the gain-bandwidth product  $GBW$  to insure the desired phase margin. The non-dominant pole is given

$$\omega_p = \frac{G_{m3}}{C_3}, \quad (3.5)$$

where  $C_3$  is given by

$$C_3 = 2(C_{GS3} + C_{GB3}) \quad (3.6)$$

Assuming that  $M_{3a}$ - $M_{3b}$  are in saturation, the gate-to-source capacitance  $C_{GS3}$  is given by

$$C_{GS3} \cong W_3 L_3 C_{ox} \cdot c_{gsi} + C_{GSon} \cdot W_3, \quad (3.7)$$

where  $C_{GSon}$  is the gate-to-source overlap capacitance per unit width for nMOS transistors.  $c_{gsi}$  is the intrinsic gate-to-source capacitance normalized to the total gate capacitance  $W L C_{ox}$ , which is typically equal to 2/3 in strong inversion and is proportionnal to  $IC$  in weak inversion.

The gate-to-bulk capacitance  $C_{GB3}$  is given by

$$C_{GB3} \cong W_3 L_3 C_{ox} \cdot c_{gbi} + C_{GBon} \cdot W_3, \quad (3.8)$$

where  $C_{GBon}$  is the gate-to-bulk overlap capacitance per unit width and  $c_{gbi}$  is the gate-to-bulk intrinsic capacitance normalized to the total gate capacitance  $W L C_{ox}$  and given by

$$c_{gbi} = \frac{n-1}{n} \cdot c_{gsi}. \quad (3.9)$$

The capacitance at node 3 then scales with  $W_3$  and  $L_3$  according to

$$C_3 = W_3 L_3 \cdot C_{WL} + W_3 \cdot C_W, \quad (3.10)$$

with

$$C_{WL} = 2 C_{ox} \cdot (c_{gsi} + c_{gbi}), \quad (3.11)$$

$$C_W = 2(C_{GSon} + C_{GBon}). \quad (3.12)$$

We already have set the inversion coefficient  $IC_3 = 40.429$ , from which we can calculate  $c_{gsi} = 0.611$  and  $c_{gbi} = 0.083$ . Since the  $W/L$  has already been set by the transconductance and the current, we can derive  $W_3$  and  $L_3$  for achieving a given capacitance  $C_3$  according to

$$W_3 = \frac{-C_W \cdot W_3/L_3 + \sqrt{W_3/L_3} \cdot \sqrt{4 C_3 C_{WL} + C_W^2 \cdot W_3/L_3}}{2 C_{WL}}, \quad (3.13)$$

$$L_3 = \frac{W_3}{W_3/L_3}. \quad (3.14)$$

Setting the non-dominant pole  $f_p$  to 10 times the  $GBW$ , we get  $C_3 = 21$  fF,  $W_3 = 140$  nm and  $L_3 = 13.49 \mu m$ . We see that  $W_3$  is smaller than the minimum width. If we don't want to increase  $W_3 L_3$  and hence  $C_3$ , we need to reduce the inversion coefficient  $IC_3$ . We can find the  $IC$  such that  $W_3 = W_{min}$  for the given  $f_p$  by looking at Figure 3.1.

We get  $IC_3 = 22.9$ ,  $W_3 = 200$  nm,  $L_3 = 10.93 \mu m$ ,  $C_3 = 13.4$  fF,  $G_{m3} = 1.716 \mu A/V$  and  $I_{spec3} = 13.08$  nA. This leads to the desired ratio  $f_p/GBW = 10.0$ .

The inversion coefficient of  $M_{3a}$ - $M_{3b}$  is therefore reduced from 40.4 to 22.9 in order to maintain a reasonable parasitic capacitance at node 3 to make sure that  $f_p$  is 10 times higher than the  $GBW$ .

Note that the  $V_{GS3}$  voltage has also dropped to  $V_{GS3} = 787$  mV, so that the quiescent output voltage is now lower than  $V_{outq} = V_{DD}/2 = 900$  mV. We might need to introduce an offset voltage to shift the output back to  $V_{outq}$  (in the high gain region). On the other hand the saturation voltage is now also lower  $V_{DSsat3} = 269$  mV improving the output swing.

 


Figure 3.1: Length  $L_3$  and width  $W_3$  of  $M_3$  versus  $IC_3$  for a given  $f_{p3}/GBW$  ratio.

### 3.5 Sizing of $M_{4a}$ - $M_{4b}$ and $M_{5a}$ - $M_{5b}$

The cascode transistors are sized according to the desired DC gain given by

$$A_{dc} = \frac{G_{m1}}{G_o} \quad (3.15)$$

where  $G_o$  is the conductance at the output node given by

$$G_o \cong G_{o35} + G_{o124} \quad (3.16)$$

where

$$G_{o35} \triangleq \frac{G_{ds3} G_{ds5}}{G_{ms5}}, \quad (3.17)$$

$$G_{o124} \triangleq \frac{(G_{ds1} + G_{ds2}) G_{ds4}}{G_{ms4}}. \quad (3.18)$$

The minimum DC gain specification is given by  $A_{dc} = 1.0e+05$  or  $A_{dc} = 100$  dB. We can then deduce the total output conductance  $G_o = 69.618$  pA/V. We will split the output conductance  $G_o$  equally between  $G_{o35}$  and  $G_{o124}$ s.

To minimize the saturation voltage and maximize the current efficiency, the cascode transistors  $M_{4a}$ - $M_{4b}$  and  $M_{5a}$ - $M_{5b}$  are biased in weak inversion. We choose their inversion coefficient as  $IC_4 = IC_5 = 0.1$ , which gives a saturation voltage  $V_{DSsat4} = V_{DSsat5} = 105$  mV. Having set the inversion coefficient and knowing the bias current, we can deduce the specific current  $I_{spec4} = 3.0$   $\mu$ A and the aspect ratio  $W_4/L_4 = 17.328$  for  $M_{4a}$ - $M_{4b}$  and  $I_{spec5} = 3.0$   $\mu$ A and  $W_5/L_5 = 4.196$  for  $M_{5a}$ - $M_{5b}$ .

We can now calculate the source transconductances that are needed for the calculation of the output conductances  $G_{ms4} = 10.621$   $\mu$ A/V and  $G_{ms5} = 10.621$   $\mu$ A/V. Having already the length of  $M_{3a}$ - $M_{3b}$ , we can estimate its output conductance  $G_{ds3} = 1.372$  nA/V. We can then deduce the output conductance of  $M_{5a}$ - $M_{5b}$   $G_{ds5} = 269.4$  nA/V, which corresponds to a cascode gain  $G_{ms5}/G_{ds5} = 39.4$ . We can then deduce the length of  $M_{5a}$ - $M_{5b}$  from  $G_{ds5}$  as  $L_5 = 56$  nm, which is lower than  $L_{min}$ .

We could choose  $L_5 = L_{min}$ , but in order to avoid DIBL and secure the DC gain, we increase the length of  $M_{5a}$ - $M_{5b}$  to  $L_5 = 540$  nm. Keeping the same  $W/L$  we get the width  $W_5 = 2.27$   $\mu$ m.

We can recalculate the contribution of  $M_{3a}$ - $M_{3b}$  and  $M_{5a}$ - $M_{5b}$  to the total output conductance  $G_{o35} = 3.6 \text{ pA/V}$  and deduce the remaining contribution allocated to  $M_{1a}$ - $M_{1b}$ ,  $M_{2b}$ - $M_{2c}$  and  $M_{4a}$ - $M_{4b}$   $G_{o124} = 0.1 \text{ nA/V}$ .

At this point we don't know the lengths neither of  $M_{1a}$ - $M_{1b}$  nor of  $M_{2b}$ - $M_{2c}$  and  $M_{4a}$ - $M_{4b}$ . We can choose that  $G_{ds1} + G_{ds2} = G_{ds4}$  and  $G_{ds1} = G_{ds2}$  so that  $G_{ds1} = G_{ds2} = G_{ds4}/2$ . We can then deduce the output conductance of  $M_{4a}$ - $M_{4b}$   $G_{ds4} = 26.316 \text{ nA/V}$  from which we get the length  $L_4 = 570 \text{ nm}$  and width  $W_4 = 9.88 \text{ }\mu\text{m}$ . The cascode voltage gain is then given by  $G_{ms4}/G_{ds4} = 403.6$ . We can deduce the length of  $M_{1a}$ - $M_{1b}$  and  $M_{2b}$ - $M_{2c}$  accounting for the different currents flowing in  $M_{4a}$ - $M_{4b}$ ,  $M_{1a}$ - $M_{1b}$  and  $M_{2b}$ - $M_{2c}$   $L_1 = 0.94 \text{ }\mu\text{m}$  and  $L_2 = 2.08 \text{ }\mu\text{m}$ .

We can now finalize the sizing of  $M_{1a}$ - $M_{1b}$  with  $W_1 = 3.29 \text{ }\mu\text{m}$ . We can check the theoretical DC gain  $A_{dc} = 1.0\text{e}+05$  (estimation) or  $A_{dc} = 100 \text{ dB}$  (estimation).

### 3.6 Sizing of $M_{2a}$ - $M_{2b}$ - $M_{2c}$

To size  $M_{2b}$ - $M_{2c}$  we will choose its saturation voltage to  $V_{SDsat2} = 300 \text{ mV}$  in order to maximize the output swing. This leads to an inversion coefficient  $IC_2 = 29.606$ , a specific current  $I_{spec2} = 0.019 \text{ }\mu\text{A}$  and an aspect ratio  $W_2/L_2 = 0.107$ . Knowing  $L_2 = 2.08 \text{ }\mu\text{m}$  we deduce  $W_2 = 220 \text{ nm}$ .

The contribution to the input-referred noise PSD of  $M_{2b}$ - $M_{2c}$  can be quite large compared to that of the differential pair  $M_{1a}$ - $M_{1b}$  because the current  $I_{b2}$  is at least two times  $I_{b1}$ . It is therefore hard to make  $G_{m2}$  much smaller than  $G_{m1}$  without drastically increasing  $IC$  and hence  $V_{DSsat}$  and loosing output swing. We can check the contribution of  $M_{2a}$ - $M_{2b}$ - $M_{2c}$  to the input-referred noise. If  $M_{2a}$ - $M_{2b}$ - $M_{2c}$  are perfectly matched, the noise produced by  $M_{2a}$  is canceled out at the output and can therefore be neglected. Since the noise is usually dominated by the flicker noise we can calculate the contribution of  $M_{2b}$ - $M_{2c}$  to the input-referred flicker noise relative to the contribution of the differential pair  $M_{1a}$ - $M_{1b}$

$$\eta_{fl}|_{M_{2b}-M_{2c}} = \frac{\rho_p}{\rho_n} \left( \frac{G_{m2}}{G_{m1}} \right)^2 \frac{W_1 L_1}{W_2 L_2} \quad (3.19)$$

We get  $\eta_{fl}|_{M_{2b}-M_{2c}} = 6.693$  which is very large.

Setting  $\eta_{fl}|_{M_{2b}-M_{2c}}$  to 1, results in  $W_2 = 0.63 \text{ }\mu\text{m}$  and  $L_2 = 5.86 \text{ }\mu\text{m}$  which reduces  $\eta_{fl}|_{M_{2b}-M_{2c}}$  to 0.930 when accounting for the effective width and length.

We can also check the contribution of  $M_{3a}$ - $M_{3b}$  to the input-referred noise by calculating

$$\eta_{fl}|_{M_{3a}-M_{3b}} = \left( \frac{G_{m3}}{G_{m1}} \right)^2 \frac{W_1 L_1}{W_3 L_3} \quad (3.20)$$

which is equal to 0.170.

### 3.7 Sizing $M_{7a}$ - $M_{7b}$

The size of  $M_{7a}$ - $M_{7b}$  is conditioned by the minimum input common-mode voltage  $V_{ic,min}$

$$V_{ic,min} = V_{GS1} + V_{DSsat7}. \quad (3.21)$$

The gate-to-source voltage  $V_{GS1}$  is given by

$$V_{GS1} = V_{T0n} + (n_{0n} - 1) V_{S1} + n_{0n} U_T (v_p - v_s) \quad (3.22)$$

Unfortunately, at this point we don't know the value of the source voltage  $V_{S1}$  of  $M_{1a}$ - $M_{1b}$  (voltage at common-source node 1). In weak inversion  $v_p - v_s \cong 0$  so that

$$V_{GS1} \cong V_{T0n} + (n_{0n} - 1) V_{S1} \quad (3.23)$$

Since we don't know  $V_{S1}$  we can approximate  $V_{GS1}$  by  $V_{T0n} = 455 \text{ mV}$ . If we set the minimum input common-mode voltage to  $V_{ic,min} = 0.75 \text{ V}$ , it results in a saturation voltage for  $M_{7a}$ - $M_{7b}$  equal to  $V_{DSsat7} = 295 \text{ mV}$ , which corresponds to an inversion coefficient  $IC_7 = 28.5$ . Having the  $IC$  and the current we can derive the specific current  $I_{spec7} = 18 \text{ nA}$  and the aspect ratio  $W_7/L_7 = 0.025$ . Since the  $W/L$  is small, we need to set the width to  $W_7 = W_{min} = 200 \text{ nm}$  resulting in a length  $L_7 = 8.15 \text{ }\mu\text{m}$ .

We now need to set the bias voltages  $V_{b1}$  and  $V_{b2}$ .

### 3.8 Bias voltages $V_{b1}$ and $V_{b2}$

We still need to calculate the required bias voltages  $V_{b1}$  for  $M_{5a}$ - $M_{5b}$  and  $V_{b2}$  for  $M_{4a}$ - $M_{4b}$ .

We start calculating the maximum bias voltage  $V_{b2,max}$  still keeping  $M_{2a}$ - $M_{2b}$  in saturation

$$V_{b2,max} = V_{DD} - V_{SG4} - V_{SDsat2} \quad (3.24)$$

The saturation voltage of  $M_{2a}$ - $M_{2b}$  is given by  $IC_2$  as  $V_{SDsat2} = 300 \text{ mV}$ . The source-to-gate voltage  $V_{SG4}$  is given by

$$V_{SG4} = V_{T0p} + (n_{0p} - 1) V_{BS4} + n_{0p} U_T (v_p - v_s) \quad (3.25)$$

In weak inversion  $v_p - v_s \cong 0$  and therefore

$$V_{SG4} \cong V_{T0p} + (n_{0p} - 1) V_{BS4} \quad (3.26)$$

However, at this point we don't know the source voltage of  $M_{4a}$ - $M_{4b}$ . We can estimate that  $V_{SG4} \cong V_{T0p} = 445 \text{ mV}$  which results in  $V_{b2,max} = 1055 \text{ mV}$ .

We also want to make sure that the  $V_{SD}$  voltage across  $M_{4a}$ - $M_{4b}$  is large enough not to degrade the output conductance. We can choose  $V_{SD4} = 200 \text{ mV}$ , which gives  $V_{b2,min} = 542 \text{ mV}$ .

The maximum value of  $V_{b1}$  is set by keeping a sufficient  $V_{DS}$  voltage for  $M_{5a}$ - $M_{5b}$

$$V_{b1,max} = V_{GS5} - V_{DS5} + V_{GS3} \quad (3.27)$$

where

$$V_{GS5} = V_{T0n} + (n_{0n} - 1) V_{SB5} + n_{0n} U_T (v_p - v_s) \cong V_{T0n} + (n_{0n} - 1) V_{SB5} \cong V_{T0n}. \quad (3.28)$$

If we choose  $V_{DS5} = 200 \text{ mV}$ , we get  $V_{b1,max} = 1042 \text{ mV}$ .

The minimum  $V_{b1}$  voltage is set by keeping  $M_{3a}$ - $M_{3b}$  in saturation

$$V_{b1,min} = V_{GS5} + V_{DSsat3} \quad (3.29)$$

resulting in  $V_{b1,min} = 724 \text{ mV}$ .

So the bias voltages  $V_{b1}$  and  $V_{b2}$  should satisfy the following inequalities

$$0.724 \text{ V} \leq V_{b1} \leq 1.042 \text{ V} \text{ and}$$

$$0.542 \text{ V} \leq V_{b2} \leq 1.055 \text{ V}$$

We finally choose  $V_{b1} = 1.000 \text{ V}$  and  $V_{b2} = 0.600 \text{ V}$ .

The sizing process is now completed. The transistor sizes and bias are summarized below.

### 3.9 Summary

#### 3.9.1 Specifications

The specifications are recalled in Table 3.5.

Table 3.5: OTA specifications.

Specification	Symbol	Value	Unit
Minimum DC gain	$A_{dc}$	100	$dB$
Minimum gain-bandwidth product	$GBW$	1	$MHz$
Load capacitance	$C_L$	1	$pF$
Maximum input-referred random offset voltage	$V_{os}$	10	$mV$
Phase margin	$PM$	60	$^\circ$

#### 3.9.2 Bias

The bias information are summarized in Table 3.6.

Table 3.6: OTA bias.

Bias voltage or current	Symbol	Value	Unit
Supply voltage	$V_{DD}$	1.80	$V$
Bias current	$I_{b1}$	250.00	$nA$
Bias current	$I_{b2}$	550.00	$nA$
Cascode bias voltage	$V_{b1}$	1.00	$V$
Cascode bias voltage	$V_{b2}$	0.60	$V$

#### 3.9.3 Transistor information

The transistor sizes and large-signal variables are summarized in Table 3.7, whereas Table 3.8 gives the small-signal and thermal noise parameters. An Excel table is generated with more information (e.g. all the parasitic capacitances).

Table 3.7: Transistor size and bias information.

Transistor	$W$ [ $\mu m$ ]	$L$ [ $\mu m$ ]	$I_D$ [ $nA$ ]	$I_{spec}$ [ $nA$ ]	$IC$	$V_G - V_{T0}$ [ $mV$ ]	$V_{DSsat}$ [ $mV$ ]
M1a	3.29	0.94	250	2503	0.1	-45	105
M1b	3.29	0.94	250	2503	0.1	-45	105
M2a	1.26	5.86	1100	37	29.5	228	300
M2b	0.63	5.86	550	19	29.5	228	300
M2c	0.63	5.86	550	19	29.5	228	300
M3a	0.20	10.93	300	13	22.9	205	269
M3b	0.20	10.93	300	13	22.9	205	269
M4a	9.88	0.57	300	3001	0.1	-44	105
M4b	9.88	0.57	300	3001	0.1	-44	105
M5a	2.27	0.54	300	3006	0.1	-45	105
M5b	2.27	0.54	300	3006	0.1	-45	105
M7a	0.20	8.15	500	18	28.5	230	295
M7b	0.20	8.15	500	18	28.5	230	295



Table 3.8: Transistor small-signal and thermal noise parameters.

Transistor	n	$G_{spec} [\mu A/V]$	$G_{ms} [\mu A/V]$	$G_m [\mu A/V]$	$G_{ds} [nA/V]$	$\gamma_n$
M1a	1.271	96.716	8.852	6.962	13.298	0.653
M1b	1.271	96.716	8.852	6.962	13.298	0.653
M2a	1.306	1.439	7.134	5.463	9.386	0.834
M2b	1.306	0.719	3.567	2.731	4.693	0.834
M2c	1.306	0.719	3.567	2.731	4.693	0.834
M3a	1.271	0.506	2.182	1.716	1.372	0.808
M3b	1.271	0.506	2.182	1.716	1.372	0.808
M4a	1.306	115.980	10.621	8.133	26.316	0.671
M4b	1.306	115.980	10.621	8.133	26.316	0.671
M5a	1.271	116.161	10.623	8.355	27.778	0.653
M5b	1.271	116.161	10.623	8.355	27.778	0.653
M7a	1.271	0.678	3.297	2.593	3.067	0.811
M7b	1.271	0.678	3.297	2.593	3.067	0.811

## 4 OTA Characteristics

In this section, we check whether the specs are achieved.

### 4.1 Open-loop gain

We can calculate the various OTA features related to the open-loop transfer function, which are given in Table 4.1.

Table 4.1: OTA gain variables.

Symbol	Theoretical Value	Unit
$A_{dc}$	103.201	$dB$
$G_{m1}$	6.962	$\mu A/V$
$G_{m2}$	2.731	$\mu A/V$
$G_{m3}$	1.716	$\mu A/V$
$G_{ms4}$	10.621	$\mu A/V$
$G_{ms5}$	10.623	$\mu A/V$
$G_{ds1}$	13.298	$nA/V$
$G_{ds2}$	4.693	$nA/V$
$G_{ds3}$	1.372	$nA/V$
$G_{ds4}$	26.316	$nA/V$
$G_{ds5}$	27.778	$nA/V$
$C_3$	25.217	$fF$
$C_4$	54.747	$fF$
$f_0$	7.530	$Hz$
$GBW$	1.089	$MHz$
$f_p$	10.830	$MHz$
$f_z$	21.660	$MHz$
$f_{p4}$	30.877	$MHz$

The gain-bandwidth product from the specifications is repeated here

$GBW = 1.000 \text{ MHz}$  (from spec).

The estimate value assuming that all the non-dominant poles are much higher than the  $GBW$  is given by

$GBW_{est} = 1.089 \text{ MHz}$  (estimation).

The  $GBW$  accounting for the effect of the additional non-dominant poles is given by

$GBW_{the} = 1.084 \text{ MHz}$  (theory).

We see that there is only a small difference between  $GBW_{est}$  and  $GBW_{the}$ , which confirms that the non-dominant poles are sufficiently far from  $GBW$  as stated in Table 4.1.

We can now plot the gain response Using the variables given in Table 4.1. It is shown in Figure 4.1.

From Figure 4.1, we see that the  $GBW$  and DC gain are met.

 


Figure 4.1: OTA theoretical transfer function.

We can now have a look at the input-referred noise PSD.

## 4.2 Input-referred noise

We can now compute all the parameters needed for the calculation of the OTA thermal noise excess factor and its input-referred thermal noise PSD and resistance. They are given in Table 4.2.

Table 4.2: OTA thermal noise parameters.

Symbol	Theoretical Value	Unit
$G_{m1}$	6.962	$\mu A/V$
$G_{m2}$	2.731	$\mu A/V$
$G_{m3}$	1.716	$\mu A/V$
$G_{m1}/G_{m2}$	2.549	-
$G_{m1}/G_{m3}$	4.057	-
$\gamma_{n1}$	0.653	-
$\gamma_{n2}$	0.834	-
$\gamma_{n3}$	0.808	-
$\eta_{th}$	0.805	-
$\gamma_{ota}$	2.359	-
$R_{nt}$	338.892	$k\Omega$
$S_{ninth}$	5.6e-15	$V^2/Hz$
$\sqrt{S_{ninth}}$	74.914	$nV/\sqrt{Hz}$
$10 \cdot \log(S_{ninth})$	-142.509	$dBv/\sqrt{Hz}$

From Table 4.2, we see that the contribution of  $M_{2b}$ - $M_{2c}$  and  $M_{3a}$ - $M_{3b}$  is only 0.805 that of  $M_{1a}$ - $M_{1b}$ . This leads to an OTA thermal noise excess factor  $\gamma_{n,ota} = 2.359$ , which is 1.8 times larger than that of the differential pair  $2\gamma_{n1} = 1.307$ .

We can now compute all the parameters needed for the calculation of the input-referred flicker noise and the corner frequency. They are given in Table 4.3.

Table 4.3: OTA flicker noise parameters.

Symbol	Theoretical Value	Unit
$(G_{m1}/G_{m2})^2$	6.5	-
$(G_{m1}/G_{m3})^2$	16.5	-
$\rho_p/\rho_n$	8.3	-
$\frac{W_1 \cdot L_1}{W_2 \cdot L_2}$	0.7	-
$\frac{W_1 \cdot L_1}{W_3 \cdot L_3}$	1.1	-
$\eta_{fl}$	0.999	-
$\sqrt{S_{nin,fl}(1\text{ Hz})}$	36.5	$\mu V/\sqrt{\text{Hz}}$
$10 \cdot \log(S_{nin,fl}(1\text{ Hz}))$	-88.7	$\text{dBV}/\sqrt{\text{Hz}}$
$f_k$	238	$\text{kHz}$

As desired, from Table 4.3, we see that the contribution of  $M_{2b}$ - $M_{2c}$  and  $M_{3a}$ - $M_{3b}$  to the flicker noise is only 0.999 that of  $M_{1a}$ - $M_{1b}$ . It is slightly lower than the value obtained in the design phase simply because the calculations use the effective width and length.

We can plot the input-referred noise which is shown in Figure 4.2.

 


Figure 4.2: OTA theoretical input-referred noise PSD.

### 4.3 Input-referred offset

The variance of the input-referred offset voltage is given by (2.32), which is repeated below

$$\sigma_{V_{os}}^2 = \sigma_{V_T}^2 + \sigma_{\beta}^2. \quad (4.1)$$

$\sigma_{V_T}^2$  is the  $V_T$ -mismatch given by

$$\sigma_{V_T}^2 = \sigma_{V_{T1}}^2 \cdot (1 + \xi_{V_T}) \quad (4.2)$$

where

$$\xi_{VT} = \left( \frac{G_{m2}}{G_{m1}} \right)^2 \left( \frac{A_{V_{Tp}}}{A_{V_{Tp}}} \right)^2 \frac{W_1 L_1}{W_2 L_2} + \left( \frac{G_{m3}}{G_{m1}} \right)^2 \frac{W_1 L_1}{W_3 L_3} \quad (4.3)$$

represents the  $V_T$ -mismatch contributions to the input-referred offset of the current source  $M_{2b}$ - $M_{2c}$  and current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair.

$\sigma_\beta^2$  is the  $\beta$ -mismatch given by

$$\sigma_\beta^2 = \left( \frac{I_{b1}}{G_{m1}} \right)^2 \cdot \sigma_{\beta_1}^2 \cdot (1 + \xi_\beta) \quad (4.4)$$

where

$$\xi_\beta = \left( \frac{I_{b2}}{I_{b1}} \right)^2 \left( \frac{A_{\beta_p}}{A_{\beta_n}} \right)^2 \frac{W_1 L_1}{W_2 L_2} + \left( \frac{I_{b3}}{I_{b1}} \right)^2 \frac{W_1 L_1}{W_2 L_2}. \quad (4.5)$$

The parameter for calculating the standard deviation of the input-referred offset voltage are given in Table 4.4.

Table 4.4: OTA input-referred offset parameters.

Symbol	Theoretical Value	Unit
$\sigma_{VT1}$	2.843	$mV$
$\sigma_{VT2}$	2.602	$mV$
$\sigma_{VT3}$	3.382	$mV$
$\sigma_{\beta_1}$	0.569	%
$\sigma_{\beta_2}$	0.520	%
$\sigma_{\beta_3}$	0.676	%
$(G_{m2}/G_{m1})^2$	0.154	-
$(G_{m3}/G_{m1})^2$	0.061	-
$W_1 L_1/(W_2 L_2)$	0.838	-
$W_1 L_1/(W_3 L_3)$	1.415	-
$(I_{b2}/I_{b1})^2$	4.840	-
$(I_{b3}/I_{b1})^2$	1.440	-
$\xi_{VT}$	0.215	-
$\xi_\beta$	6.092	-
$\sigma_{VT}^2$	9.821	$mV^2$
$\sigma_{VT}$	3.134	$mV$
$\sigma_\beta^2$	0.296	$mV^2$
$\sigma_\beta$	0.544	$mV$
$\sigma_{Vos}$	3.181	$mV$

From Table 4.4 and contrary to the other OTA, we see that in the case of the folded cascode OTA the  $\beta$ -mismatch cannot be neglected. This is mostly because of the  $W_1 L_1/(W_3 L_3)$  ratio equal to 1.415.

## 4.4 Current and power consumption

The total current consumption, ignoring the current drawn by  $M_{2a}$  and  $M_{7a}$ , is  $I_{tot} = 2I_{b2} = 1.1 \mu A$  and the power consumption is  $P = 1.980 \mu W$ .

Assuming the input differential pair  $M_{1a}$ - $M_{1b}$  is biased in deep weak inversion, the minimum bias current  $I_{b1,min}$  is directly related to the gain-bandwidth product  $GBW$  according to

$$I_{b1,min} \cong nU_T \cdot C_L \cdot \omega_u = nU_T \cdot C_L \cdot 2\pi GBW, \quad (4.6)$$

which is equal to  $207\text{ nA}$ . The minimum total current consumption assuming  $\alpha \triangleq I_{b3}/I_{b1} = 1.2$  can then be estimated as  $I_{tot,min} \cong 2I_{b2,min} = 2(I_{b1,min} + I_{b3,min}) = 2I_{b1,min}(1 + \alpha) = 909\text{ nA}$ . The actual current consumption accounting for some margin taken on the  $GBW$  is therefore 21% higher than the minimum.

The current consumption of the folded cascode OTA is 2.2 times larger than that of the telescopic OTA for the same specifications.

**i** Note

Note that the telescopic OTA is the differential OTA that has the minimum power consumption for similar gain-bandwidth product, DC gain and phase margin specifications. Of course it has the smallest input and output voltage swings.

The above design will now be checked against simulations.

## 5 Simulation results from ngspice

The theoretical results can be validated with the results obtained from simulations performed with ngspice. In order to run the simulations you need to have ngspice correctly installed. Please refer to the installation instructions.

### **i** Note

The simulations are performed with ngspice [2] using the EKV 2.6 compact model [4] [3] [11]. For ngspice, we use the original Verilog-A implementation of EKV 2.6 [6] modified by C. Enz to get the operating point informations and available on the Gitub va-models site provided by D. Warning at [5] [12]. The Verilog-A code was then compiled with OpenVAF [13] to generate the OSDI for running it with ngspice. The parameters correspond to a generic 180 nm bulk CMOS process [7].

### 5.1 Operating point

We first write the parameter file for this specific design for running the ngspice simulations. Before running the AC and NOISE simulations, we first need to check the quiescent voltages and currents and the operating points of all transistors by running a .OP simulation.

Table 5.1: OTA node voltages with the OTA in open-loop without offset correction.

Node	Voltage
vdd	1.8
vb1	1
vb2	0.6
inp	0.9
inn	0.9
out	0.785397
ic	0.9
id	0
1	0.391179
2	0.930824
3	0.785397
4	1.18638
5	1.18638
6	0.462576
7	0.462576
8	0.813271

We can extract the OTA quiescent node voltages from the ngspice .ic file. They are presented in Table 5.1. We see that the simulated quiescent output voltage is  $V_{outq} = 785 \text{ mV}$ . This is fine and the OTA is biased in the high gain region. Similarly to the telescopic OTA, the quiescent output voltage is actually set by the  $V_{GS}$  voltage of  $M_{3a}$ . Indeed, if perfect matching is assumed (which is the case in

the simulation), since M<sub>5a</sub>-M<sub>5b</sub> have the same drain current and share the same gate voltage, they have the same  $V_{GS}$  voltage and also have the same drain voltage. We therefore don't need to extract any offset voltage at this point and can proceed with the simulation of the large-signal characteristic.

The operating point information for all transistors are extracted from the ngspice .op file. The data is split into the large-signal operating informations in Table 5.2, the small-signal operating point informations in Table 5.3 and the noise operating point informations in Table 5.4.

Table 5.2: Operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D$ [nA]	$I_{spec}$ [nA]	$IC$	$n$	$V_{Dsat}$ [mV]
M1a	249	2539	0.098	1.27	120
M1b	249	2539	0.098	1.27	120
M2a	1100	32	33.992	1.31	405
M2b	572	17	33.988	1.31	405
M2c	572	17	33.988	1.31	405
M3a	323	14	23.420	1.27	354
M3b	323	14	23.420	1.27	354
M4a	323	2738	0.118	1.31	121
M4b	323	2738	0.118	1.31	121
M5a	323	3216	0.100	1.27	120
M5b	323	3216	0.100	1.27	120
M7a	500	18	27.292	1.27	374
M7b	499	18	27.282	1.27	374

Table 5.3: Small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$G_m$ [ $\mu A/V$ ]	$G_{ms}$ [ $\mu A/V$ ]	$G_{ds}$ [nA/V]
M1a	7.105	8.816	13.317
M1b	7.105	8.816	13.317
M2a	4.845	6.584	3.794
M2b	2.519	3.424	2.239
M2c	2.519	3.424	2.239
M3a	1.759	2.268	1.493
M3b	1.759	2.268	1.493
M4a	8.975	11.266	23.312
M4b	8.975	11.266	23.312
M5a	9.230	11.371	46.171
M5b	9.230	11.371	46.171
M7a	2.538	3.272	1.645
M7b	2.522	3.267	16.297

Table 5.4: Noise operating point information extracted from ngspice .op file for each transistor.

Transistor	$R_n$ [k $\Omega$ ]	$\sqrt{S_{ID,th}}$ [nA/ $\sqrt{Hz}$ ]	$\gamma_n$ [-]	$\sqrt{S_{ID,fl}}$ at 1Hz [nA/ $\sqrt{Hz}$ ]
M1a	90.681	38.770	0.644	18245
M1b	90.681	38.770	0.644	18245
M2a	184.599	55.317	0.894	32389.5
M2b	354.989	76.709	0.894	44892.6
M2c	354.989	76.709	0.894	44892.6
M3a	481.883	89.374	0.848	19211.6



Table 5.4: Noise operating point information extracted from ngspice .op file for each transistor.

Transistor	$R_n [k\Omega]$	$\sqrt{S_{ID,th}} [nA/\sqrt{Hz}]$	$\gamma_n [-]$	$\sqrt{S_{ID,fl}} \text{ at } 1\text{Hz} [nA/\sqrt{Hz}]$
M3b	481.883	89.374	0.848	19211.6
M4a	72.719	34.719	0.653	40159.7
M4b	72.719	34.719	0.653	40159.7
M5a	69.428	33.924	0.641	29894.2
M5b	69.428	33.924	0.641	29894.2
M7a	336.221	74.654	0.853	22274.8
M7b	340.070	75.080	0.858	22274.8

We can also check the bias voltages and operating region of each transistor which are given in Table 5.5.

Table 5.5: Bias voltages and operating regions extracted from ngspice for each transistor.

Trans.	Type	Funct.	$V_G [V]$	$V_S [V]$	$V_D [V]$	$V_{DS} [mV]$	$V_{DSsat} [mV]$	Reg.	Sat.
M1a	n	DP	0.900	0.391	1.186	795	120	WI	sat
M1b	n	DP	0.900	0.391	1.186	795	120	WI	sat
M2a	p	CM	0.869	0.000	0.869	869	405	SI	sat
M2b	p	CM	0.869	0.000	0.614	614	405	SI	sat
M2c	p	CM	0.869	0.000	0.614	614	405	SI	sat
M3a	n	CM	0.785	0.000	0.463	463	354	SI	sat
M3b	n	CM	0.785	0.000	0.463	463	354	SI	sat
M4a	p	CA	1.200	0.614	1.015	401	121	MI	sat
M4b	p	CA	1.200	0.614	1.015	401	121	MI	sat
M5a	n	CA	1.000	0.463	0.785	323	120	MI	sat
M5b	n	CA	1.000	0.463	0.785	323	120	MI	sat
M7a	n	CM	0.813	0.000	0.813	813	374	SI	sat
M7b	n	CM	0.813	0.000	0.391	391	374	SI	sat

From Table 5.2, we see that all transistors have a sufficiently large  $V_{DS}$  voltage and are therefore biased in saturation. Additionnally we see that all the saturation voltages in the output current branch M2d, M4, M7 and M3b are summing up to 1000 mV leaving an output voltage swing about equal to  $V_{out,swing} \cong 800 \text{ mV}$ . This output voltage swing could be increased by about 250 mV by biasing M2d and M3b in weak inversion. This would be at the cost of larger transistors and a less current matching in the current mirrors.

From Table 5.5, we see that all transistors are biased in saturation. The operating points look fine. We can now proceed with the simulation of the open-loop large-signal transfer characteristic.

## 5.2 Large-signal differential transfer characteristic

We now simulate the DC differential transfer characteristic. The simulation of the large-signal input-output characteristic is presented in Figure 5.1.

From Figure 5.1, we see that the output swing is about  $V_{out,swing} = 400 \text{ mV}$ , which is even smaller than the above estimation. We can now zoom into the high gain region in order to extract the offset voltage that is needed to bring the output voltage back to  $V_{outq} = 0.900 \text{ V}$ . The simulation results are presented in Figure 5.2.

 


Figure 5.1: Simulated large-signal input-output characteristic.

 


Figure 5.2: Zoom of the simulated large-signal input-output characteristic in the gain region.

We can now save the extracted offset voltage  $V_{os} = 0.624 \mu V$  that is required to bring the output voltage to  $V_{outq} = 0.900 V$  and that will be used for the following .AC and .NOISE simulations.

### 5.3 Open-loop gain

After having checked the operating point information and making sure that the OTA output is not saturated by extracting the required offset voltage for bringing the output operating point to the desired value  $V_{outq} = 0.900 V$ , we can now perform the AC simulation.

 


Figure 5.3: Simulated gain response compared to theoretical estimation.

From Figure 5.3, we see that the simulated transfer function is very close to the theoretical estimation below the  $GBW$ . The simulated gain-bandwidth product  $GBW = 1.116 MHz$  is equal to the theoretical estimation  $1.084 MHz$  and slightly above target  $1.000 MHz$ . The simulated DC gain  $A_{dc} = 105.131 dB$  is slightly higher than the estimated DC gain  $103.201 dB$  and higher than the specifications  $100 dB$ , offering some margin. Notice that the DC gain obtained from the AC simulation is consistent with the value extracted above from the DC transfer characteristic.

We now will have a look at the input-referred noise power spectral density (PSD).

### 5.4 Input-referred noise

The simulated input-referred noise PSD is presented in Figure 5.4 and compared to the theoretical estimation.

From Figure 5.4, we see a perfect match between simulation and theoretical estimation for both the flicker and the white noise except above the  $GBW$  where the simulated noise PSD becomes larger than

 


Figure 5.4: Simulated input-referred noise PSD compared to theoretical estimation.

the theoretical estimation. This is simply due to the fact that the theoretical input-referred noise PSD has been obtained by dividing the output current noise by the square of the equivalent transconductance without accounting for the frequency dependence occurring above the  $GBW$ .

The individual contributions of the various transistors to the input-referred white noise PSD are detailed in Figure 5.5 and compared to the theoretical white noise.

 


Figure 5.5: Breakdown of the contributions to the simulated input-referred white noise PSD.

From Figure 5.5, we can observe a perfect match of the total input-referred white noise PSD between simulation and the theoretical estimation below the  $GBW$ . The white noise is dominated by the differential pair  $M_{1a}$ - $M_{1b}$  which is  $1 + \eta_{th} = 1.819$  times (or 2.598 dB) lower than the total white noise. The contribution of  $M_{2a}$ - $M_{2b}$ - $M_{2c}$  is about 2.031 times (or 3.078 dB) lower than the contribution of  $M_{1a}$ - $M_{1b}$ . Note that it is mostly  $M_{2b}$ - $M_{2c}$  that contribute since the contribution of  $M_{2a}$  is a common mode signal that is cancelled at the output if we assume perfect matching. The contribution of  $M_{3a}$ - $M_{3b}$  is about 3.062 times (or 4.860 dB) lower than the contribution of  $M_{1a}$ - $M_{1b}$ . Finally, the contributions of the cascode transistors  $M_4$  and  $M_5$  are completely negligible. (56.128 dB lower for  $M_4$  and 76.521 dB lower for  $M_5$ ). This confirms that the noise of the cascode transistors  $M_4$  and  $M_5$  can be totally

neglected in the above analysis.

The simulated value of  $\eta_{th} = 0.819$  is close to the theoretical estimation  $\eta_{th} = 0.805$ . Finally, the simulated OTA thermal noise excess factor  $\gamma_{n,ota} = 2.349$  is about equal to the predicted value  $\gamma_{n,ota} = 2.359$ .

Figure 5.6 presents the breakdown of the contributions of the various transistors to the input-referred flicker noise.

 


Figure 5.6: Breakdown of the contributions to the simulated input-referred flicker noise PSD.

Similarly to the white noise, Figure 5.6 shows that the total simulated input-referred flicker noise PSD perfectly matches the theoretical prediction. We can observe  $M_{2a}$ - $M_{2b}$ - $M_{2c}$  have a slightly less contribution than  $M_{1a}$ - $M_{1b}$ . This is confirmed by the value of  $\eta_{fl} = 0.830$  ( $-0.812$  in  $dB$ ) which is slightly lower than the theoretical value  $\eta_{fl} = 0.999$ . The contribution of  $M_{3a}$ - $M_{3b}$  is  $11.666$   $dB$  lower than the contribution of  $M_{1a}$ - $M_{1b}$ . Finally, the contributions of the cascode transistors  $M_{4a}$ - $M_{4b}$  and  $M_{5a}$ - $M_{5b}$  are completely negligible.

The contributions of the various transistors to the total input-referred noise PSD is shown in Figure 5.7.

## 5.5 Input common-mode voltage range

We can check the input common-mode voltage range by connecting the OTA as a voltage follower and sweeping the positive input.

As shown in Figure 5.8, the output follows the input voltage from  $0.34$   $V$  up to  $1.50$   $V$ . So the input common-mode voltage range is about  $1.16$   $V$ .

## 5.6 Step-response

In this section we will check the step response of the OTA operating as a voltage follower as shown in Figure 5.9 with its output connected to the negative input and with the same load capacitance  $C_L = 1$   $pF$ .

 


Figure 5.7: Breakdown of the contributions to the simulated input-referred noise PSD.

 


Figure 5.8: Simulated input common-mode voltage range.

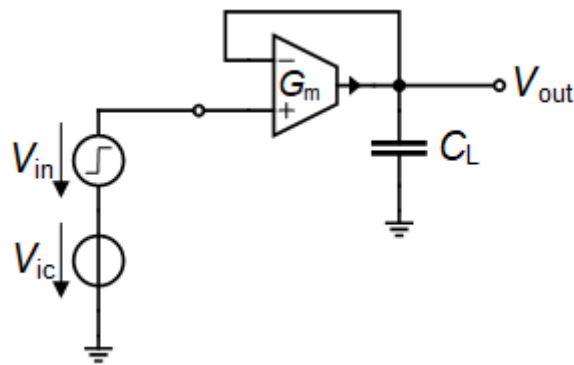


Figure 5.9: Schematic of the OTA connected as a voltage follower.

### 5.6.1 Small-step

According to the input common-mode voltage range established above, we will set the input common-mode voltage to  $V_{ic} = 0.900 \text{ V}$  to make sure that the OTA is in the high gain region. We start by imposing a small step  $\Delta V_{in} = 10 \text{ mV}$  on top of a common mode voltage  $V_{ic} = 0.900 \text{ V}$ . The simulation results are shown in Figure 5.10 where  $\Delta V_{in}(t) \triangleq V_{in+}(t) - V_{ic}$  and  $\Delta V_{out}(t) \triangleq V_{out}(t) - V_{outq}$  with  $V_{outq} \cong V_{ic}$  is the quiescent output voltage.  $\Delta V_{in}$  and  $\Delta V_{out}$  are compared to the response of a single pole circuit having a cut-off frequency equal to the  $GBW$ . From Figure 5.10, we see that the simulation result is very close to the first-order response.

 


Figure 5.10: Step response of the OTA connected as a voltage follower for a small input step.

### 5.6.2 Large step

The simulation results for a larger step  $\Delta V_{in} = 300 \text{ mV}$  are shown in Figure 5.11 where  $\Delta V_{in}(t) \triangleq V_{in+}(t) - V_{ic}$  and  $\Delta V_{out}(t) \triangleq V_{out}(t) - V_{outq}$  with  $V_{outq} \cong V_{ic}$  is the quiescent output voltage.  $\Delta V_{in}$  and  $\Delta V_{out}$  are compared to the response of a single pole circuit having a cut-off frequency equal to the  $GBW$ . We now observe the effect of slew-rate which increases the settling time.

## 5.7 Current and power consumption

The total current consumption, ignoring the current drawn by  $M_{2a}$  and  $M_{7a}$ , is  $I_{tot} = 2I_{b2} = 1.1 \mu\text{A}$  and the power consumption is  $P = 1.980 \mu\text{W}$ .

Assuming the input differential pair  $M_{1a}$ - $M_{1b}$  is biased in deep weak inversion, the minimum bias current  $I_{b1,min}$  is directly related to the gain-bandwidth product  $GBW$  according to

$$I_{b1,min} \cong nU_T \cdot C_L \cdot \omega_u = nU_T \cdot C_L \cdot 2\pi GBW, \quad (5.1)$$

which is equal to  $207 \text{ nA}$ . The minimum total current consumption assuming  $\alpha \triangleq I_{b3}/I_{b1} = 1.2$  can then be estimated as  $I_{tot,min} \cong 2I_{b2,min} = 2(I_{b1,min} + I_{b3,min}) = 2I_{b1,min}(1 + \alpha) = 909 \text{ nA}$ . The actual current consumption accounting for some margin taken on the  $GBW$  is therefore 21% higher than the minimum.

The current consumption of the folded cascode OTA is 2.2 times larger than that of the telescopic OTA for the same specifications.

 


Figure 5.11: Step response of the OTA connected as a voltage follower for a large input step highlighting the slew-rate effect.

**i** Note

Note that the telescopic OTA is the differential OTA that has the minimum power consumption for similar gain-bandwidth product, DC gain and phase margin specifications. Of course it has the smallest input and output voltage swings.



## 6 Conclusion

This notebook presented the analysis, design and verification of the folded-cascode OTA [1] designed for a generic 180nm bulk CMOS process. The detailed analysis provided all the equations that were then used in the design phase to reach the target specifications. The design was then performed using the inversion coefficient approach with the sEKV transistor model [11] [14] [15]. The theoretical performance resulting from the design were then evaluated.

The design was then verified by simulation using ngspice [2] with the EKV 2.6 compact model [4] and the parameters of a generic 180 nm bulk CMOS process. After carefully checking the operating point, the large-signal transfer characteristic was simulated. The small-signal open-loop transfer function was then simulated making sure the OTA was biased in the high gain region. The simulated transfer function was very close to the theoretical prediction except for the DC gain which is slightly smaller but still in spec. The simulations have also shown that the gain-bandwidth product  $GBW$  and the DC gain specifications are both achieved.

The input-referred noise was then simulated. The total simulated input-referred noise PSD perfectly matches the theoretical estimation for both the white noise and the flicker noise. The contributions of the various transistors to the input-referred white noise were then extracted from the noise simulation and compared to the theoretical estimation. It was shown that the total white noise is very close to the theoretical estimation. The simulation of the input-referred flicker noise have shown that it is dominated by the input differential pair  $M_{1a}$ - $M_{1b}$  and the current sources  $M_{2b}$ - $M_{2c}$ . Finally, the simulations have confirmed that the noise contributions of the cascode transistors are completely negligible.

The input common-mode voltage range was then simulated with the OTA connected as a voltage follower. The common-mode input voltage is ranging from 0.34 V to 1.50 V.

Finally, the small-signal step response was simulated and successfully compared to the response of a single-pole system. The step-response with a large input step highlighted the effect of slew-rate.

The folded cascode OTA is easier to design than the telescopic OTA, because of the relaxed voltage constraints. It can reach higher DC gain and output voltage swing at the cost of more noise.

# References

- [1] T. C. Choi, R. T. Kaneshiro, R. W. Brodersen, P. R. Gray, W. B. Jett, and M. Wilcox, “High-frequency CMOS switched-capacitor filters for communications application,” *IEEE Journal of Solid-State Circuits*, vol. 18, no. 6, pp. 652–664, 1983, doi: [10.1109/JSSC.1983.1052015](https://doi.org/10.1109/JSSC.1983.1052015).
- [2] Holger Vogt, Giles Atkinson, Paolo Nenzi, “Ngspice User’s Manual Version 43.” <https://ngspice.sourceforge.io/docs/ngspice-43-manual.pdf>, 2024.
- [3] C. C. Enz, F. Krummenacher, and E. A. Vittoz, “An Analytical MOS Transistor Model Valid in All Regions of Operation and Dedicated to Low-Voltage and Low-Current Applications,” *Analog Integrated Circuits and Signal Processing Journal*, vol. 8. [https://github.com/chrisenz/EKV/tree/main/EKV2.6/docs/EKV\\_original\\_paper\\_1995\\_prepub.pdf](https://github.com/chrisenz/EKV/tree/main/EKV2.6/docs/EKV_original_paper_1995_prepub.pdf), pp. 83–114, 1995.
- [4] M. Bucher, C. Lallement, C. Enz, F. Théodoloz, and F. Krummenacher, “The EPFL-EKV MOSFET Model Equations for Simulation.” [https://github.com/chrisenz/EKV/blob/main/EKV2.6/docs/ekv\\_v26\\_rev2.pdf](https://github.com/chrisenz/EKV/blob/main/EKV2.6/docs/ekv_v26_rev2.pdf), 1998.
- [5] M. Bucher, C. Lallement, C. Enz, F. Théodoloz, and F. Krummenacher, “EKV 2.6 Verilog-A Code.” <https://github.com/chrisenz/EKV/tree/main/EKV2.6/va/code>, 2024.
- [6] W. Grabinski *et al.*, “FOSS EKV2.6 verilog-a compact MOSFET model,” in *European solid-state device research conference (ESSDERC)*, 2019, pp. 190–193. doi: [10.1109/ESSDERC.2019.8901822](https://doi.org/10.1109/ESSDERC.2019.8901822).
- [7] W. Grabinski *et al.*, “FOSS EKV 2.6 parameter extractor,” in *2015 22nd international conference mixed design of integrated circuits & systems (MIXDES)*, 2015, pp. 181–186. doi: [10.1109/MIXDES.2015.7208507](https://doi.org/10.1109/MIXDES.2015.7208507).
- [8] Han, H.-C. and A. D’Amico and C. Enz, “SEKV-E: Parameter Extractor of Simplified EKV I-V model for Low-power Analog Circuits.” <https://gitlab.com/moscm/sekv-e>, 2022.
- [9] F. Krummenacher, E. Vittoz, and M. Degrauwe, “Class AB CMOS amplifier micropower SC filters,” *Electronics Letters*, vol. 17, no. 13, pp. 433–435, 1981.
- [10] M. G. Degrauwe, J. Rijmenants, E. A. Vittoz, and H. J. D. Man, “Adaptive biasing CMOS amplifiers,” *IEEE Journal of Solid-State Circuits*, vol. 17, no. 3, pp. 522–528, 1982.
- [11] C. C. Enz and E. A. Vittoz, *Charge-Based MOS Transistor Modeling - The EKV Model for Low-Power and RF IC Design*, 1st ed. John Wiley, 2006.
- [12] Dietmar Warning, “Verilog-A Models for Circuit Simulation.” <https://github.com/dwarning/VA-Models>, 2024.
- [13] SemiMod GmbH, “Open VAF.” <https://openvaf.semimod.de/docs/getting-started/introduction/>, 2025.
- [14] C. Enz, F. Chicco, and A. Pezzotta, “Nanoscale MOSFET Modeling: Part 1: The Simplified EKV Model for the Design of Low-Power Analog Circuits,” *IEEE Solid-State Circuits Magazine*, vol. 9, no. 3, pp. 26–35, 2017.
- [15] C. Enz, F. Chicco, and A. Pezzotta, “Nanoscale MOSFET Modeling: Part 2: Using the Inversion Coefficient as the Primary Design Parameter,” *IEEE Solid-State Circuits Magazine*, vol. 9, no. 4, pp. 73–81, 2017.